

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 9587

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. I) ODD SEMESTER THEORY

EXAMINATION 2013-14

**BASIC ELECTRICAL & ELECTRONICS
ENGINEERING**

Time : 3 Hours

Total Marks : 100

Note : Attempt **all** questions. Assume suitable data wherever necessary.


SECTION—A

1. Attempt **all** parts of this question : **(2×10=20)**
- (i) What is the condition of resonance in RLC circuit ?
 - (ii) What will be reactive power, if power factor is unity ?
 - (iii) Why armature windings are placed in rotor in DC Machine ?
 - (iv) Is single phase motor self starting ?
 - (v) What is the bias in which Zener diode works ?
 - (vi) Which is the device in which Pinch-off situation occurs ?
 - (vii) What is the decimal equivalent of BCD number 1010 1010 ?
 - (viii) Write the expression for a lamp which is controlled from two positions A and B.
 - (ix) Which is the instrument in which no eddy current and hysteresis losses occur ?
 - (x) Can voltmeter have very low internal resistance ?

SECTION—B

2. Attempt any **three** parts of the following : (10×3=30)

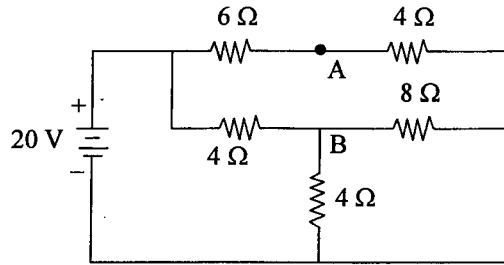(a) Determine the voltage V_{AB} in the circuit shown in the fig.



- (b) What are the differences between a DC shunt motor and a DC series motor ?
- (c) Explain the principle of electromechanical energy conversion.
- (d) Explain the working principle of capacitor start and capacitor run motor single phase induction motor.
- (e) Explain the p-n junction rectifier (half wave and full wave) circuit.

SECTION—C

3. Attempt any **one** part of the following : (10×1=10)

- (a) Explain the diode acts as rectifier and write the difference between Ideal Diode and Commercial Diode with the help of V-I characteristics.
- (b) Draw the structure of JFET and explain in detail the effect of gate-source voltage on the channel when :
- No bias
 - Small reverse bias and
 - Large reverse bias such that pinch-off occurs.

4. Attempt any **one** part of the following : (10×1=10)

- Explain the common base and common emitter configuration of BJT.
- Explain the clipping and clamping circuits.

5. Attempt any **two** parts of the following : (5×2=10)

(a) Simplify the Boolean function using K-map :

$$F(x, y, z) = \Sigma (0, 2, 3, 4, 6).$$

(b) Given Boolean function :

$$F = x y' z + x' y' z + w' x y + w x' y + x y z$$

- Obtain the truth table of the function.
- Draw the logic diagram using original Boolean expression.

(c) The given two binary numbers $X = 1010010$ and $Y = 1000011$, perform the subtraction (a) $X - Y$, (b) $Y - X$ using 1's complement.

6. Attempt any **two** parts of the following : (5×2=10)

- Derive the torque equation of PMMC. A PMMC Instrument with 100 turn coil has a magnetic flux density in its air gap of $B = 0.2$ T. The coil dimension are diameter (D) = 1 cm, length $l = 1.5$ cm. Calculate the torque on the coil for a current of 1 mA.
- Explain the circuit of moving Iron type Voltmeter and Ammeter.
- Explain the single phase dynamometer type wattmeter.

7. Attempt any **one** part of the following : (10×1=10)

- Describe the different type of electrical instruments.
- Explain the pinch off in JFET. Also explain the fixed biasing of JFET.